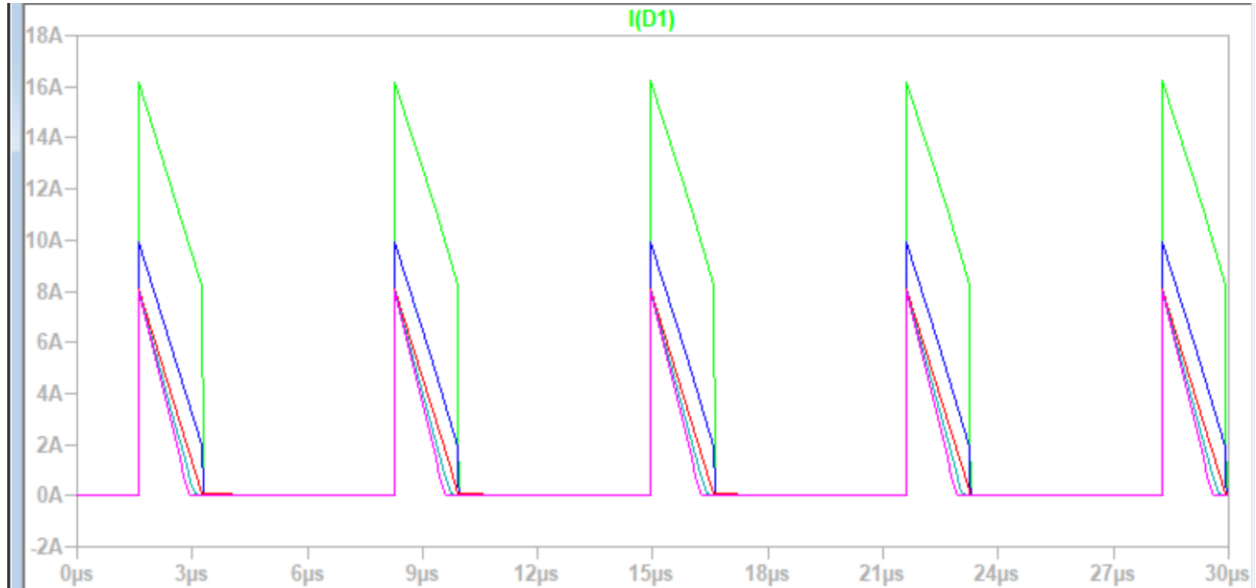


## Problem 1


- a. Using **.step** plot 5 complete cycles of the diode current  $i_D(t)$  when  $50\Omega \leq R \leq 250\Omega$ .

Diode Current when  $R_o = 50, 100, 150, 200, 250$



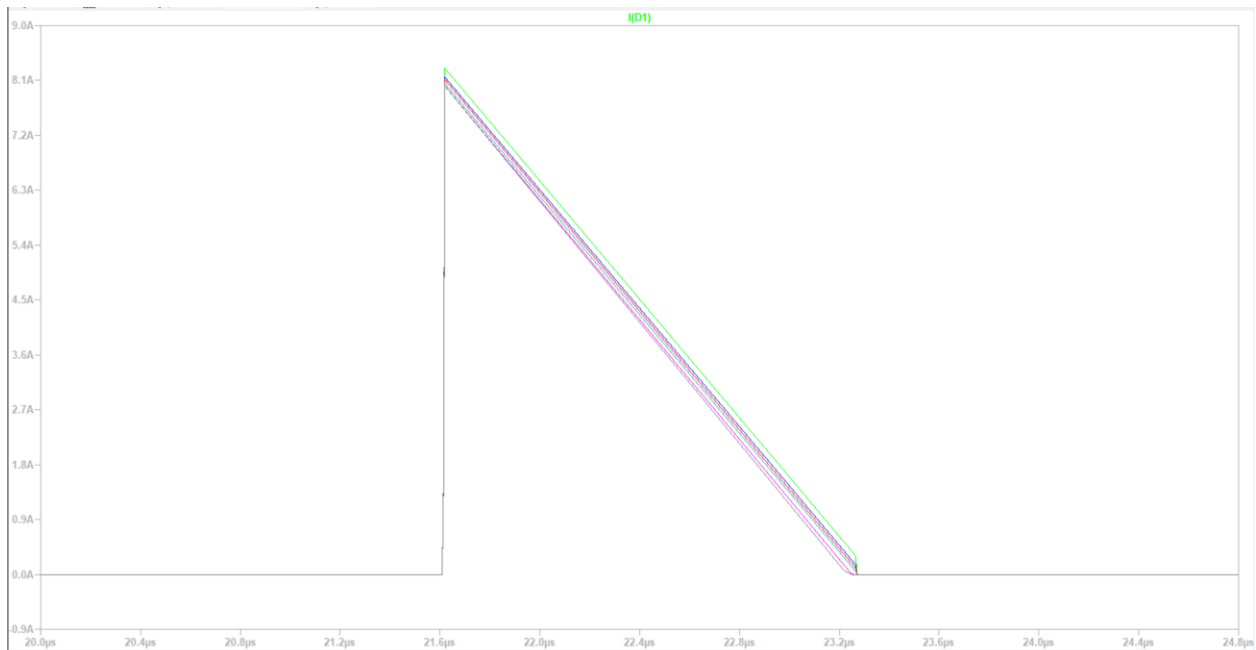
- b. In your simulation, determine the value of  $R$  that will result in the operation at the boundary between CCM and DCM for the current  $i_D(t)$ .

$R_o$  with sweep through 140, 144, 148, 152, 156, 160



Based on these pictures,  $R_o = 152$  is the boundary between CCM and DCM.

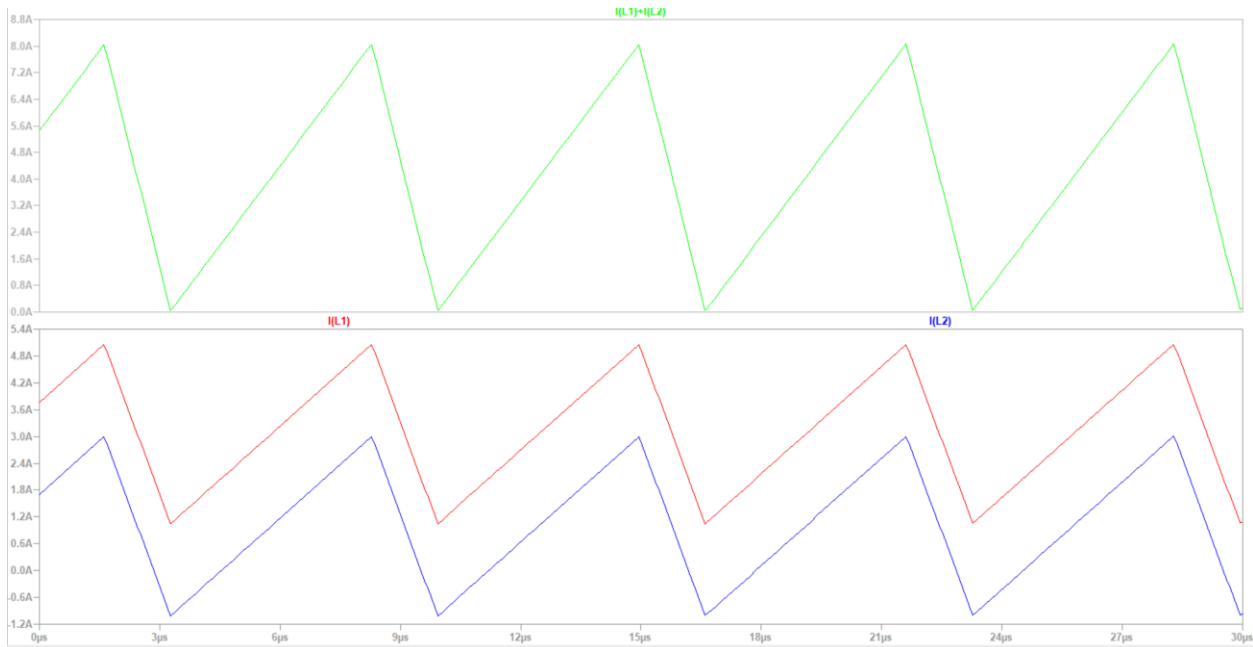
- c. Plot 5 complete cycles of the currents  $i_{L1}(t)$  and  $i_{L2}$  when the converter is operating at the boundary between CCM and DCM, and when the converter has reached periodic steady state.



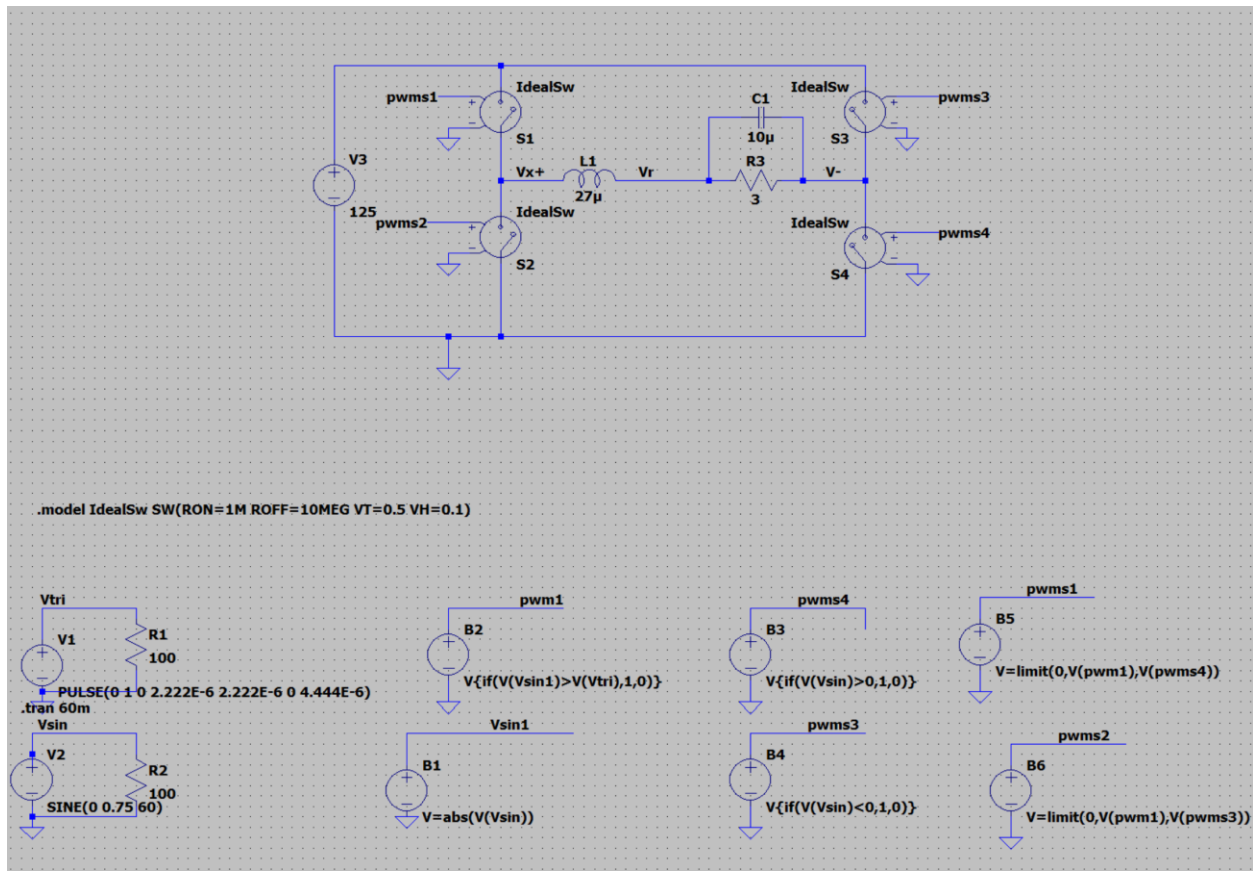
### Problem 3

Use LTSpice to simulate the inverter of [Figure 3.1](#) using a sine-triangle intercept PWM modulation.

- You can use a circuit similar to the one shown in [Figure 3.2](#) to obtain the PWM signals of the fast switching devices (S1 and S2).
- We define  $k$  as the *modulation depth*, and it is a parameter that you vary to change the amplitude of the output's fundamental.
- The parameter values are:  $V_i=125 \text{ V}$ ,  $L=27 \mu\text{H}$ ,  $C=10 \mu\text{F}$ ,  $R=3 \Omega$ , and  $f_{ac}=60 \text{ Hz}$ .




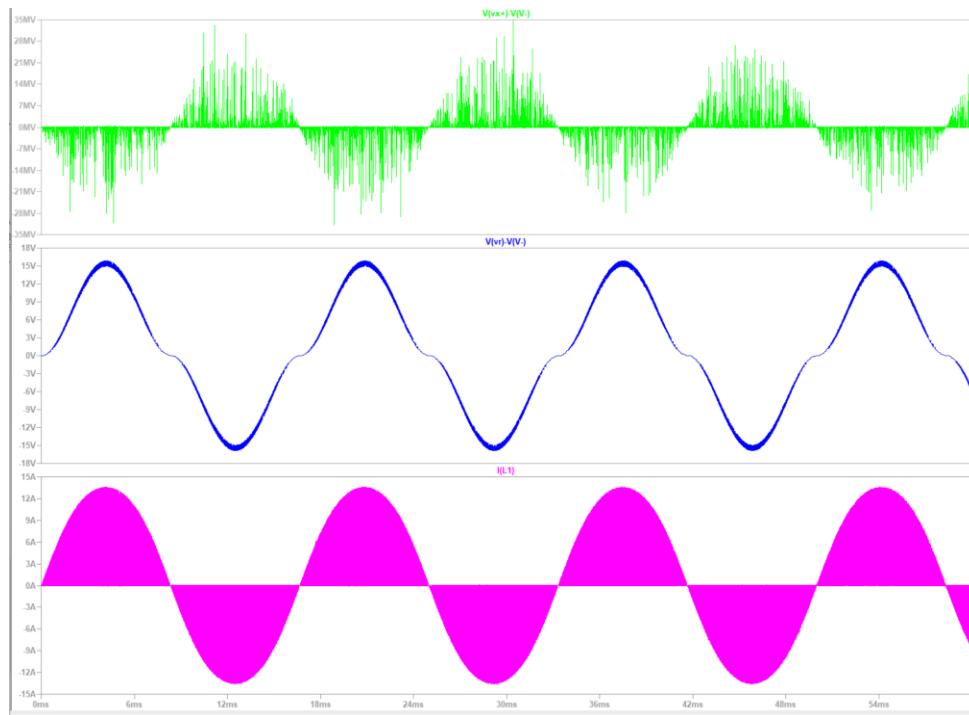- Set the frequency of the carrier triangle signal, vtr, to 225 kHz and set k=0.75.
  - Plot the inductor current  $i_x(t)$ ,  $v_x(t)$ , and the voltage across the resistive load.




- Also, plot the FFT of these signals **using at least three full ac cycles** of the corresponding waveforms to obtain the FFT.

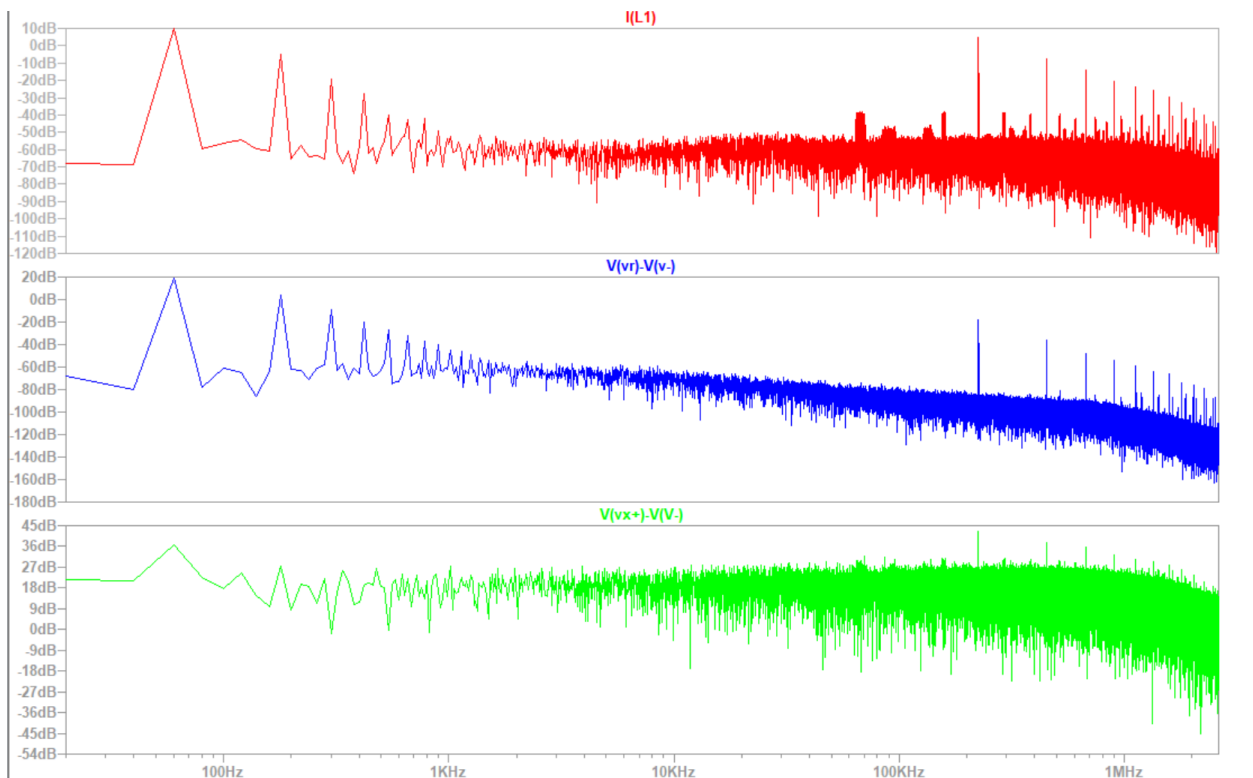As to be expected,  $V_x$  has one major peak at 60 hz, and the next major peak is at 225 kHz.


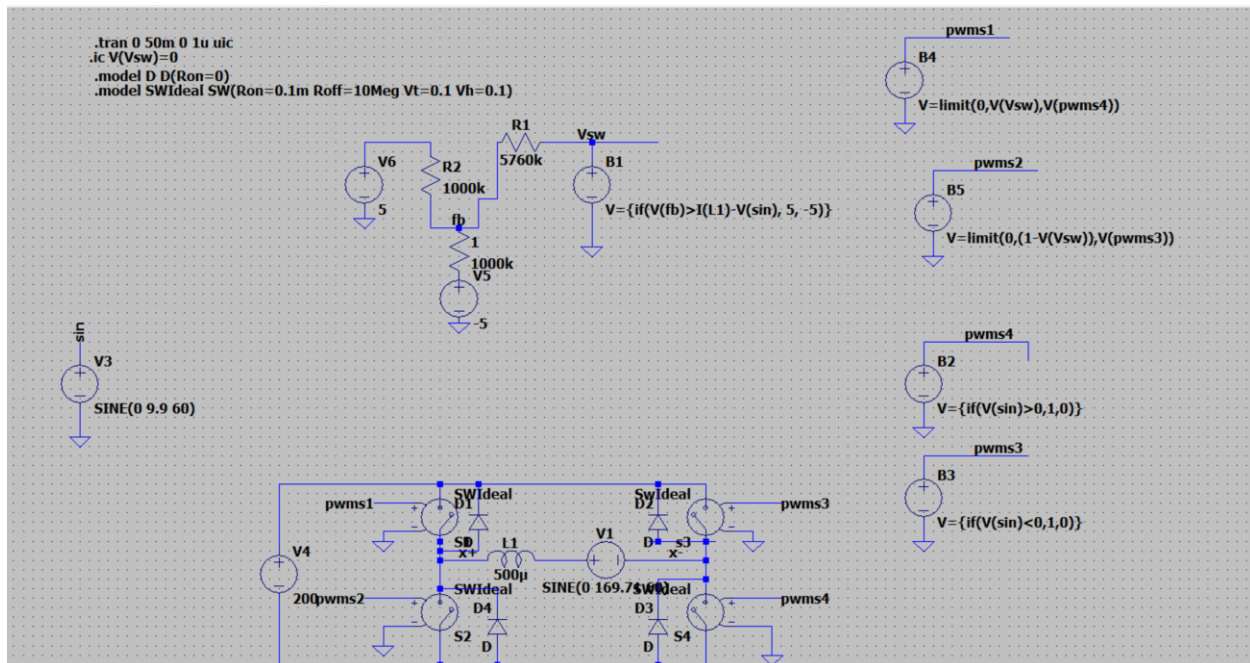
## Problem 4


- Use LTSpice to simulate an inverter supplying power to the ac line, similar to the one shown in [Figure 4.1](#). For this problem, make  $V_{ac}=120$  VRMS, 60 Hz
- Implement a hysteretic controller to regulate the inductor current, as demonstrated in [Figure 4.2](#). The inductor current should be a sine wave in phase with the ac line, with an amplitude of  $I_{ac}=7$  ARMS, and with a *hysteresis band* of  $\Delta i=0.5$  A. The input voltage,  $V_i$ , should be set to 200 Vdc. One way to establish the hysteresis band is by connecting a couple of resistors with positive feedback between the output and the input of a comparator.



- Calculate the inductor value required to achieve a maximum switching frequency of  $f_{s,max}=100$  kHz.

In the written part of the hw

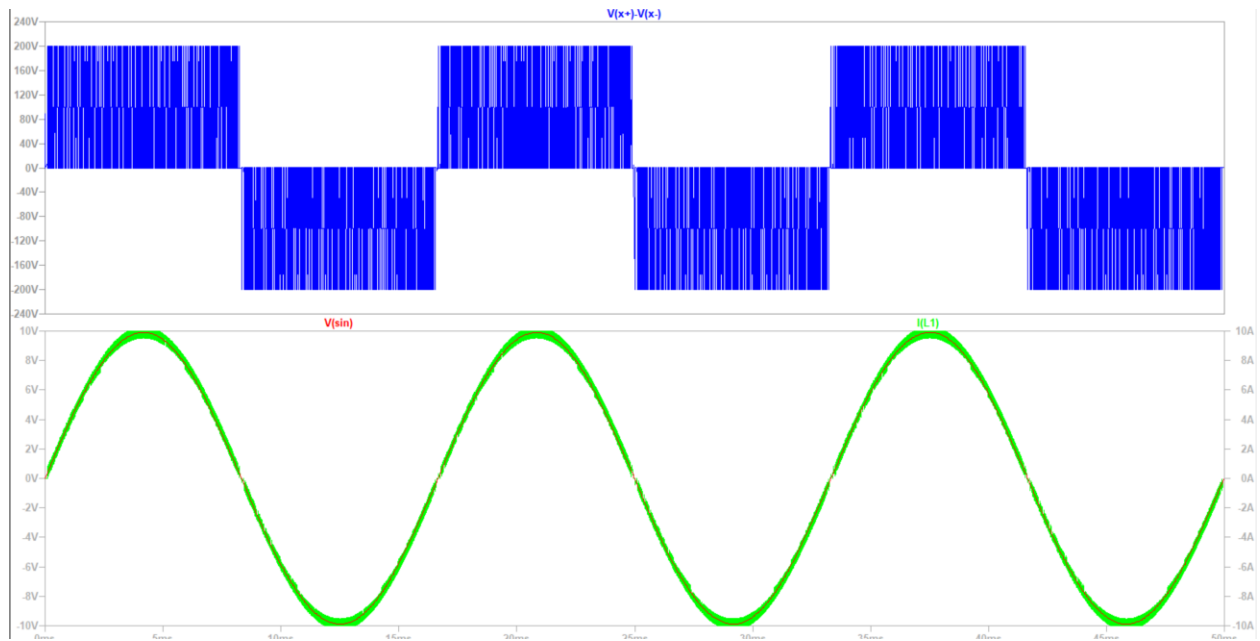Plot the time domain waveform of the output of the full bridge ( $v_x(t)$ ) and the inductor current ( $i_{ac}(t)$ ).



Additionally, plot the FFT of the waveforms. Ensure that at least three full AC cycles are used to obtain the FFT.

